

INDEX

1. FUNDAMENTAL PRINCIPLES

- ELS 1.1 The electrical circuit
- ELS 1.2 Double-throw switch
- ELS 1.3 Voltage
- ELS 1.4 Serial connection of voltage sources
- ELS 1.5 Parallel connection of voltage sources
- ELS 1.6 Current intensity
- ELS 1.7 Conductors and non-conductors
- ELS 1.8 Do liquids conduct electrical current?

2. ELECTRICAL RESISTANCE

- ELS 2.1 Ohm´s Law
 - ELS 2.1.1 Series of measurements for Ohm´s Law
- ELS 2.2 Application of Ohm´s Law
- ELS 2.3 Wires and their amount of resistance
 - ELS 2.3.1 Specific resistance of wires
- ELS 2.4 Ohmic resistor
- ELS 2.5 An incandescent lamp is not an Ohmic resistor
- ELS 2.6 Serial connection of incandescent lamps
- ELS 2.7 Serial connection of Ohmic resistors
- ELS 2.8 Voltage divider
 - ELS 2.8.1 Sliding resistor
- ELS 2.9 Parallel connection of incandescent lamps
- ELS 2.10 Parallel connection of Ohmic resistors
- ELS 2.11 Resistors in parallel and serial circuits
- ELS 2.12 Why are voltage sources connect in parallel?
- ELS 2.13 Model of a potentiometer
 - ELS 2.13.1 Dimming by means of a potentiometer
 - ELS 2.13.2 Unloaded potentiometer
 - ELS 2.13.3 Loaded potentiometer
- ELS 2.14 Internal resistance of voltage sources (terminal voltage)
- ELS 2.15 Internal resistance of a voltmeter
- ELS 2.16 Internal resistance of an ammeter
- ELS 2.17 Expansion of the measuring range of a voltmeter
- ELS 2.18 Expansion of the measuring range of an ammeter
- ELS 2.19 Wheatstone´s bridge connection

3. THERMAL ENERGY DERIVED FROM ELECTRICAL ENERGY

- ELS 3.1 Electrical energy is converted into thermal energy
- ELS 3.2 Electrical energy is converted into light energy
- ELS 3.3 Conducting wire and resistance wire
- ELS 3.4 Development of heat with different cross sections of wire
- ELS 3.5 Safety fuse

4. WORK AND POWER

- ELS 4.1 The power of incandescent lamps
- ELS 4.2 Electrical work
 - ELS 4.2.1 Heat emission and the current intensity
 - ELS 4.2.2 Electric heat equivalent
- ELS 4.3 Water equivalent

5. ELECTROCHEMISTRY

- ELS 5.1 An electrolytic element
 - ELS 5.1.1 Volta cell
- ELS 5.2 Electrolysis
- ELS 5.3 Electroplating
- ELS 5.4 Model of a lead accumulator
- ELS 5.5 Contact series

INDEX

3. THERMAL ENERGY DERIVED FROM ELECTRICAL ENERGY

- ELS 3.6 Bimetal fuse
- ELS 3.7 Bimetallic thermostat
- ELS 3.8 Bimetallic fire alarm

4. WORK AND POWER

- ELS 4.1.1 The power of an electric motor

6. ELECTROMAGNETISM

- ELS 6.1 Electrical current generates a magnetic field
- ELS 6.2 The magnetic field of a coil
- ELS 6.3 A magnetically manipulated switch
- ELS 6.4 A relay
- ELS 6.5 Relay with operating point and normal contact
- ELS 6.6 Self-opening switches
- ELS 6.7 An AC buzzer
- ELS 6.8 Model of a magnetic fuse

7. KINETIC ENERGY DERIVED FROM ELECTRIC ENERGY

- ELS 7.1 Motoric effects of electricity
- ELS 7.1.1 Lorentz' force
- ELS 7.2 Principle of the electric motor
- ELS 7.3 Model of the electric motor
- ELS 7.3.1 Direct current motor
- ELS 7.6 Model of a moving iron measuring instrument

8. ELECTROMAGNETIC INDUCTION

- ELS 8.1 Induction
- ELS 8.1.1 Induced electromotive force
- ELS 8.2 Principle of a generator
- ELS 8.3 The AC generator (internal pole generator)
- ELS 8.4 The AC generator (external pole generator)
- ELS 8.5 The DC-generator
- ELS 8.6 Generators with electromagnets
- ELS 8.6.1 Internal pole generator with electromagnet
- ELS 8.7 Induction by DC
- ELS 8.8 Transformer
- ELS 8.9 Transformer 1:1
- ELS 8.10 Unloaded transformer
- ELS 8.11 The current intensity is transformed as well
- ELS 8.12 Coils connected to DC
- ELS 8.13 Cut out peaks due to self-induction
- ELS 8.13.1 Lenz' Law
- ELS 8.13.2 Braking effect due to self-induction
- ELS 8.14 Coils connected to AC
- ELS 8.15 AC resistance of a coil
- ELS 8.16 Resistance and inductance in AC

INDEX

1. SEMICONDUCTORS

- EOS 1.1 PTC-resistor
- EOS 1.2 NTC-resistor
- EOS 1.3 Light dependent resistor (LDR)
- EOS 1.4 Measuring the luminous intensity
- EOS 1.5 VDR-resistor
- EOS 1.6 Solar cell

2. DIODES

- EOS 2.1 Silicon diode
- EOS 2.2 Forward voltage of a silicon diode
- EOS 2.2.1 Characteristic lines of semiconductor diodes
- EOS 2.3 Diodes protect meters
- EOS 2.4 Light-emitting diode (LED)
- EOS 2.4.1 Forward voltage of an LED
- EOS 2.5 Polarity indicators
- EOS 2.5.1 Polarity indicators at AC with variable frequency
- EOS 2.6 Zener diodes
- EOS 2.7 Stabilizing of voltage

3. TRANSISTORS

- EOS 3.1 Does a transistor consist of two diodes?
- EOS 3.1.1 How does a PNP-transistor behave?
- EOS 3.2 Base current makes collector current possible (NPN-transistor)
- EOS 3.2.1 Base current allows current at collector (PNP-transistor)
- EOS 3.3 The transistors as an amplifier
- EOS 3.3.1 Base connection (current amplification)
- EOS 3.3.2 Base connection (voltage amplification)
- EOS 3.3.3 Collector connection (current amplification)
- EOS 3.3.4 Collector connection (voltage amplification)
- EOS 3.3.5 Emitter connection (current amplification)
- EOS 3.3.6 Transfer characteristic of a NPN-transistor
- EOS 3.3.7 Transfer characteristic of a PNP-transistor
- EOS 3.3.8 Adjustment of the operating point
- EOS 3.3.9 Amplification free distortion due to base quiescent current
- EOS 3.4 Light triggered alarm
- EOS 3.5 Base voltage divider
- EOS 3.6 Construction of a burglar alarm by means of trip wire
- EOS 3.7 Automatic illumination
- EOS 3.8 Alarm by means of light barriers
- EOS 3.9 Fire alarm
- EOS 3.10 Electric thermometer

4. CONDENSERS

- EOS 4.1 A storage for electric charges
- EOS 4.2 A condenser supplies base current
- EOS 4.3 Capacitance
- EOS 4.3.1 Time switch
- EOS 4.4 A condenser blocks D.C
- EOS 4.5 Half-wave rectification
- EOS 4.6 Smoothing of rectified voltage
- EOS 4.7 Condensers as A.C. resistance
- EOS 4.7.1 Capacitive resistance at an A.C. of 50 Hz
- EOS 4.7.2 Capacitive resistance

INDEX

- EOS 4.8 Charged capacitors connected in series
- EOS 4.9 Capacitors connected in series (determination of capacitance)
- EOS 4.10 Parallel connection of charged capacitors
- EOS 4.11 Serial connection of AC resistors
- EOS 4.12 Ohmic resistors, coil and condenser in an A.C. circuit
- EOS 4.13 Filter

5. RECTIFICATION

- EOS 5.1 Principle of full-wave rectifying (mid-point tapping)
- EOS 5.2 Application of full-wave rectifying
- EOS 5.3 Bridge connection
- EOS 5.3.1 Bridge connection at A.C. with variable frequency

6. MULTIVIBRATOR

- EOS 6.1 Bistable multivibrator
- EOS 6.2 Discharging of a condenser
- EOS 6.3 A condenser prevents base current
- EOS 6.4 Monostable multivibrator
- EOS 6.5 Flashing circuit
- EOS 6.6 Multivibrator music
- EOS 6.7 Music controlled by light
- EOS 6.7.1 Music controlled by temperature

7. RESONANT CIRCUIT

- EOS 7.1 Principle of a resonant circuit
- EOS 7.1.1 Parallel resonant circuit
- EOS 7.1.2 Acceptor circuit
- EOS 7.2 Continuous oscillations
- EOS 7.3 LC-music

8. AMPLIFICATION

- EOS 8.1 The resistance of human bodies
- EOS 8.1.1 A transistor step controls a second step
- EOS 8.1.2 Alarm at failure of the heating
- EOS 8.2 Automatic level measuring
- EOS 8.3 Lie detector
- EOS 8.4 Microphone amplifier
- EOS 8.5 Sum and difference amplifier
- EOS 8.6 A motor armature signals its position
- EOS 8.7 Direct-current motor without commutator

9. LOGIC CIRCUITS

- EOS 9.1 The logic AND-circuit
- EOS 9.2 The logic OR-circuit
- EOS 9.3 The logic NOT-circuit
- EOS 9.4 AND-circuit
- EOS 9.5 OR-circuit
- EOS 9.6 NOT-circuit
- EOS 9.7 NAND-circuit
- EOS 9.8 NOR-circuit