

INDEX

Semiconductors – Resistors

- EL 01 NTC resistor
- EL 02 Model of an electric thermometer
- EL 03 Photo resistor (LDR)
- EL 04 Model of a light meter

Diodes

- EL 05 Silicon diode – an electric valve
- EL 06 Forward voltage of a silicon diode
- EL 07 Diodes protect measuring devices
- EL 08 Light-emitting diode (LED)
- EL 09 Forward voltage of an LED

Transistors

- EL 10 The transistor as a double diode (NPN)
- EL 11 Transistor as a switch - base current lets collector current through (NPN)
- EL 12 The transistors as an amplifier
- EL 13 Light sets off alarm
- EL 14 Base voltage divider
- EL 15 Burglar alarm with trip wire
- EL 16 Automatic illumination
- EL 17 Alarm using light barrier
- EL 18 Fire detector
- EL 19 Model of an electric thermometer
- EL 20 The conducting transistor

Capacitors

- EL 21 A capacitor can store charges
- EL 22 Direction of charging and discharging current
- EL 23 Charging a capacitor
- EL 24 Discharging a capacitor
- EL 25 Capacitor supplies base current
- EL 26 Capacitance
- EL 27 Time switch
- EL 28 A condenser blocks DC
- EL 29 Capacitor under AC voltage
- EL 30 Half-wave rectification

Multivibrator Circuit

- EL 34 Discharging of a condenser
- EL 35 A condenser prevents base current